



ENSC 450

VLSI Design - Phase 02

Daimon Gill
Siavash Rezghi
Zi Zhou Qu



For Dr. Anita Tino and Sheida Alan




Standard Cell Area and Capacitance

- Area of cell = (sum of transistor areas in cell) * (drive strength) * (unit area)
- Capacitance of cell = (single terminal input capacitance) * (drive strength) * (unit capacitance)
- Data values for worst case transitions for rise propagation delay T_{pdr}
 - NOT: "1" to "0"
 - NAND: "11" to "10"
 - NOR: "10" to "00"
 - AND: "10" to "11"

X1	NOT	NAND	NOR	AND	X4	NOT	NAND	NOR	AND
Area (μm^2)	3	8	10	11	Area (μm^2)	12	32	40	44
Gate Cap (fF)	3	4	5	4	Gate Cap (fF)	12	16	20	16

AND_X1 Results

 

Waveform Comments:

- $C_{load} = 2fF$ in Orange
- $C_{load} = 10fF$ in Blue
- Rise Transitions: '10' -> '11'
- Fall Transitions: '11' -> '10'
- Higher load capacitance results in slower transitions

```
*** parameter load = 2.000E-15 ***
*****
and_x1
***** transient analysis tnom= 25.000 temp= 125.000 *****
tpdf_1ns= 5.7701E-10 targ= 1.2077E-08 trig= 1.1500E-08
pdf_2ns= 8.2140E-10 targ= 2.4821E-08 trig= 2.4000E-08
tpdr_1ns= 6.1136E-10 targ= 6.1114E-09 trig= 5.5000E-09
pdr_2ns= 8.0889E-10 targ= 1.8809E-08 trig= 1.8000E-08
ttr_1ns= 1.0123E-10 targ= 6.1602E-09 trig= 6.0500E-09
tr_2ns= 1.1450E-10 targ= 1.8860E-08 trig= 1.8745E-09
ttr_1ns= 2.6928E-10 targ= 6.1000E-09 trig= 5.8308E-09
ttr_2ns= 3.6217E-10 targ= 1.8812E-08 trig= 1.8450E-08
**** job concluded
*** parameter load = 1.000E-14 ***
*****
and_x1
***** transient analysis tnom= 25.000 temp= 125.000 *****
tpdf_1ns= 8.7823E-10 targ= 1.2378E-08 trig= 1.1500E-08
pdf_2ns= 1.1617E-09 targ= 2.5162E-08 trig= 2.4000E-08
tpdr_1ns= 9.8153E-10 targ= 6.4815E-09 trig= 5.5000E-09
pdr_2ns= 1.2075E-09 targ= 1.9207E-08 trig= 1.8000E-08
ttr_1ns= 1.6542E-10 targ= 6.5531E-09 trig= 6.3877E-09
tr_2ns= 1.6438E-10 targ= 1.9282E-08 trig= 1.9118E-08
ttr_1ns= 6.2630E-10 targ= 6.5939E-09 trig= 5.9676E-09
ttr_2ns= 6.7341E-10 targ= 1.9321E-08 trig= 1.8648E-08
```


HSpcice Simulation:

- $T_{tran} = 1ns, C_{load} = 2fF$
- $T_{tran} = 1ns, C_{load} = 10fF$
- $T_{tran} = 2ns, C_{load} = 2fF$
- $T_{tran} = 2ns, C_{load} = 10fF$
- Collected values for T_{PDF} , T_{PDR} , T_{tr}


- X1 vs X4:
- X4 cells had expected behaviour of less delay

X1 and X1+X4 Area vs. Frequency

Area (X1+X4) (um²) vs. Frequency (MHz)

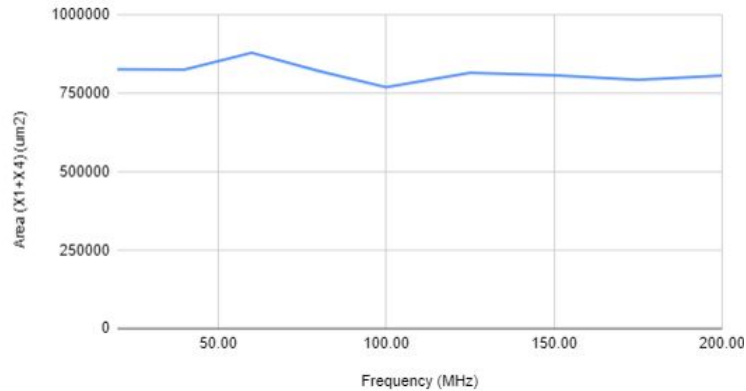

Area (X1) (um²) vs. Frequency (MHz)

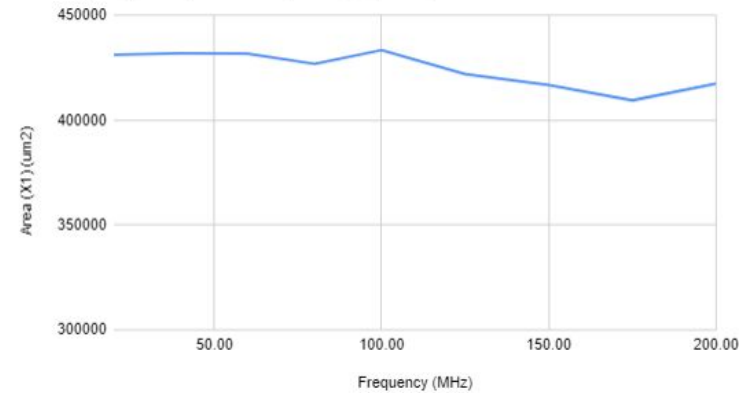

Synthesis Result Comparison

Libraries Used	FreePDK	X1 only	X1 and X4
Area (um²)	46,773	431,859	826,802
Critical Path (ns)	Slack Met (0.14)	Slack Met (0.0)	Slack Met (0.67)
Data Arrival (ns)	4.70	16.67	24.33
Period (ns)	5	16.67	25
Frequency	200 MHz	60 MHz	40 MHz